



ANALOG PHOTONIC NEEDS FOR PHASED ARRAY ANTENNAS

DARPA AOSP WORKSHOP
December 6, 2000

Dr. Akis Goutzoulis
Northrop Grumman ESSD
Antenna Department
Microwave Photonics

Analog photonic needs for REAL phased array antennas

- **Tunable front-end RF filters**

(It assumes the existence of low V_π modulators)

- **Low cost, miniaturized programmable delay lines**

- **Analog RF manifolds**


- **Analog/Digital manifolds**

(It assumes the existence of low V_π modulators)

- **Tunable optical filter banks**

Need: *Optically-implemented RF tunable filters*

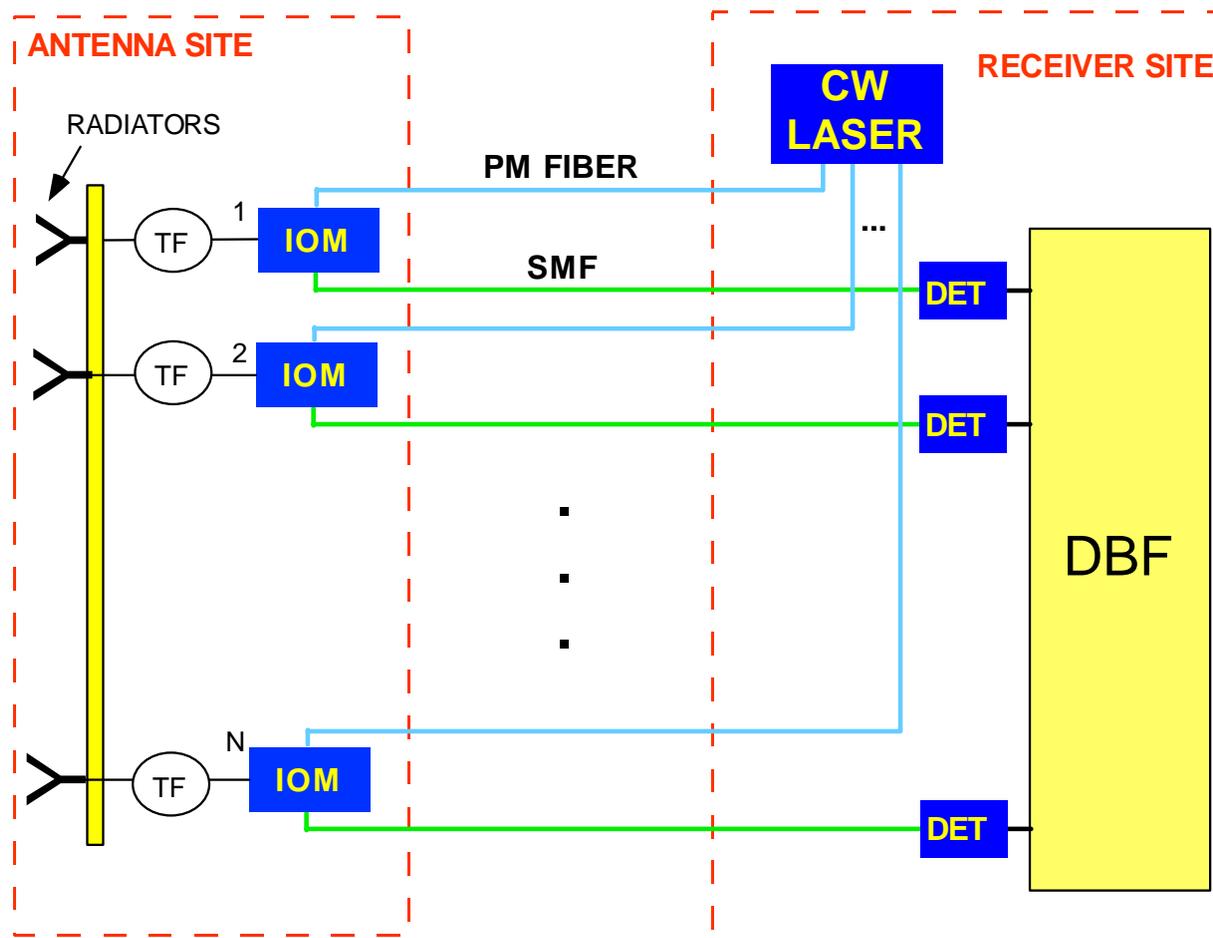
- Multi-octave systems suffer from 2nd, 3rd etc harmonic and other unwanted signals
- RF tunable filters at the front end is a must to eliminate unwanted signals and reduce ADC spurious effects
- Not an easy task for RF or MEMS technology



CAN WE MAKE A TUNABLE RF FILTER WITHIN THE IOM ???

Need: *Optically-implemented RF tunable filters*


IDEAL ALL-OPTICAL FRONT-END ARCHITECTURE

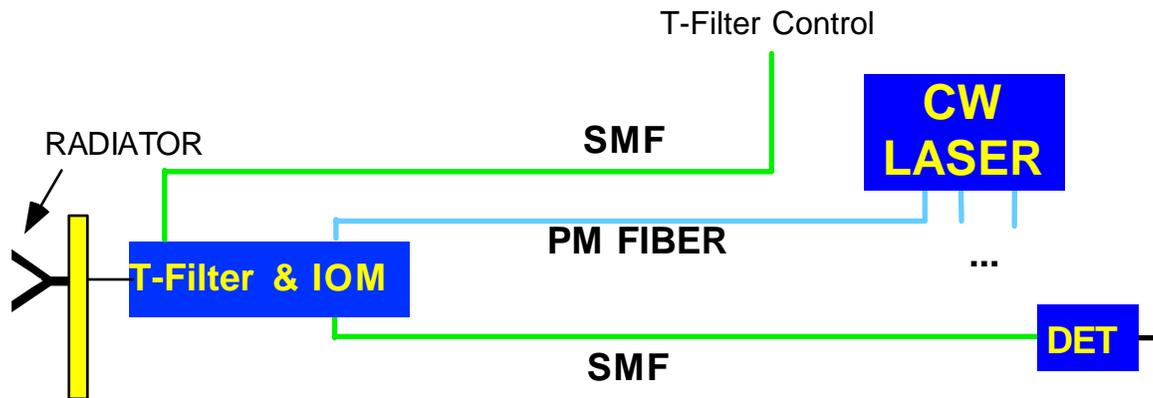



- Filter must have all-BW condition, and sub-octave tunable passband
Example for 2-18 GHz instantaneous BW
 - (1) all-BW (2-18)
 - (2) 2-4 GHz, 4-8 GHz, 8-12 GHz, 9-18 GHz
- Sub-ms speed OK
- Optical control is great (enables remoting with no wires)

Need: *Low loss optical delay lines (analog RF manifolds)*

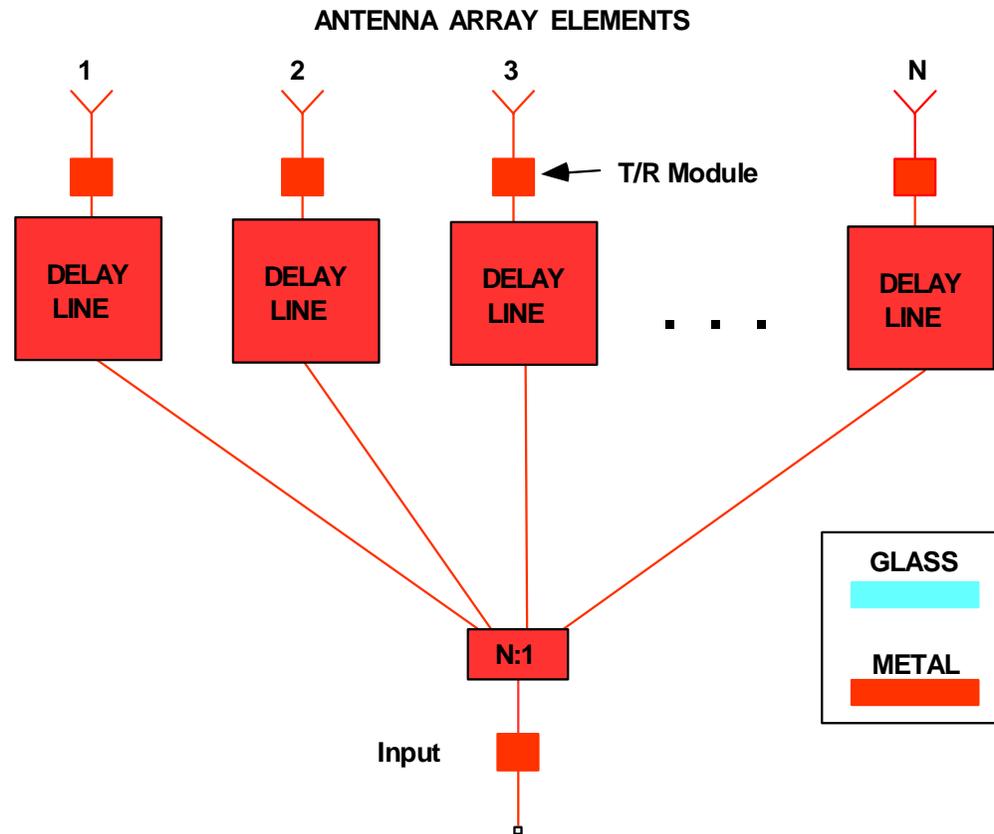For wideband (> 5 GHz) T/R antennas, it is very difficult to fabricate low cost, low loss electronic delay lines for multi-octave TTD.



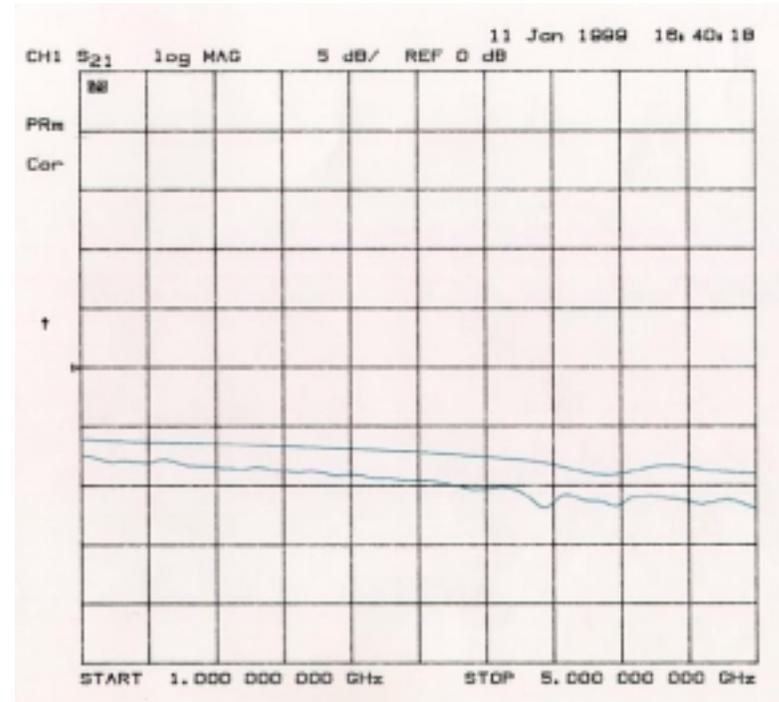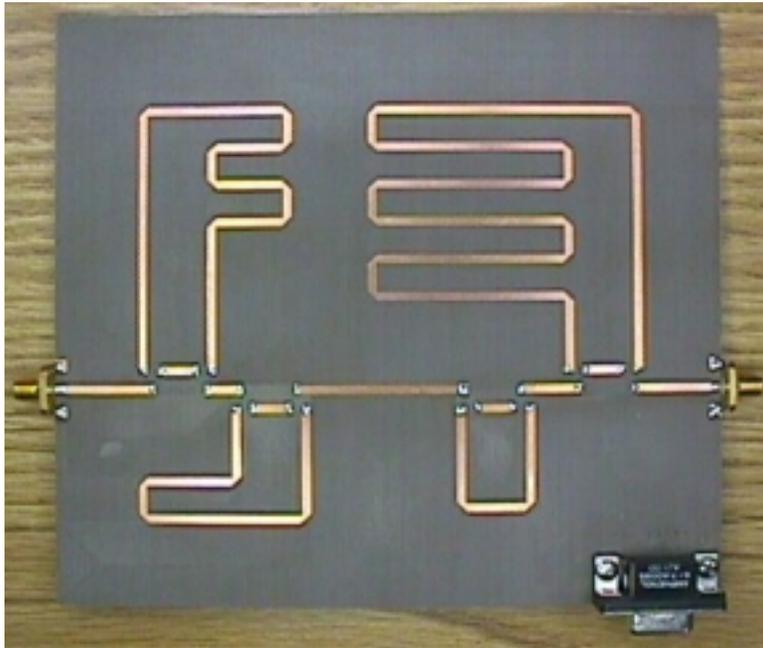Electronic bi-directional delay lines are OK up to C-band




0000

1111

- 4-bits, 3.75 ns total delay, 50 ns switching speed,
- Cost: < \$ 30 for moderate quantities (switch cost \$ 7 for small quantities)

Need: Low loss optical delay lines (analog RF manifolds)

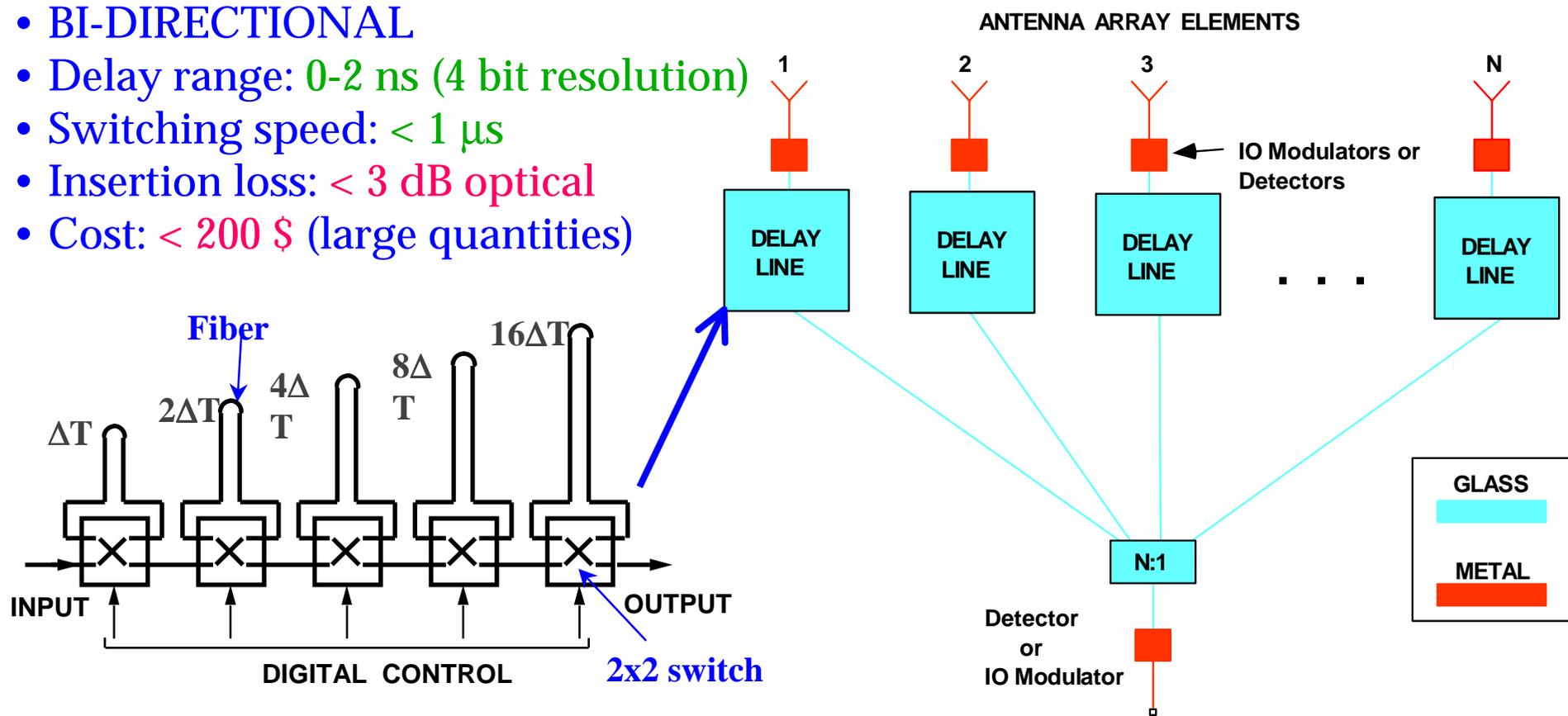
- BI-DIRECTIONAL
- Delay range: 0-2 ns (4 bit resolution)
- Switching speed: $< 1 \mu\text{s}$
- Insertion loss: $< 3 \text{ dB}$ optical
- Cost: $< 200 \text{ \$}$ (large quantities)



- Optical analog manifolds are needed for wideband transmit applications
- Can be used for "some" wideband receive applications

Need: Low loss optical delay lines (DBF/RF manifolds)


Wideband DBF manifold architecture

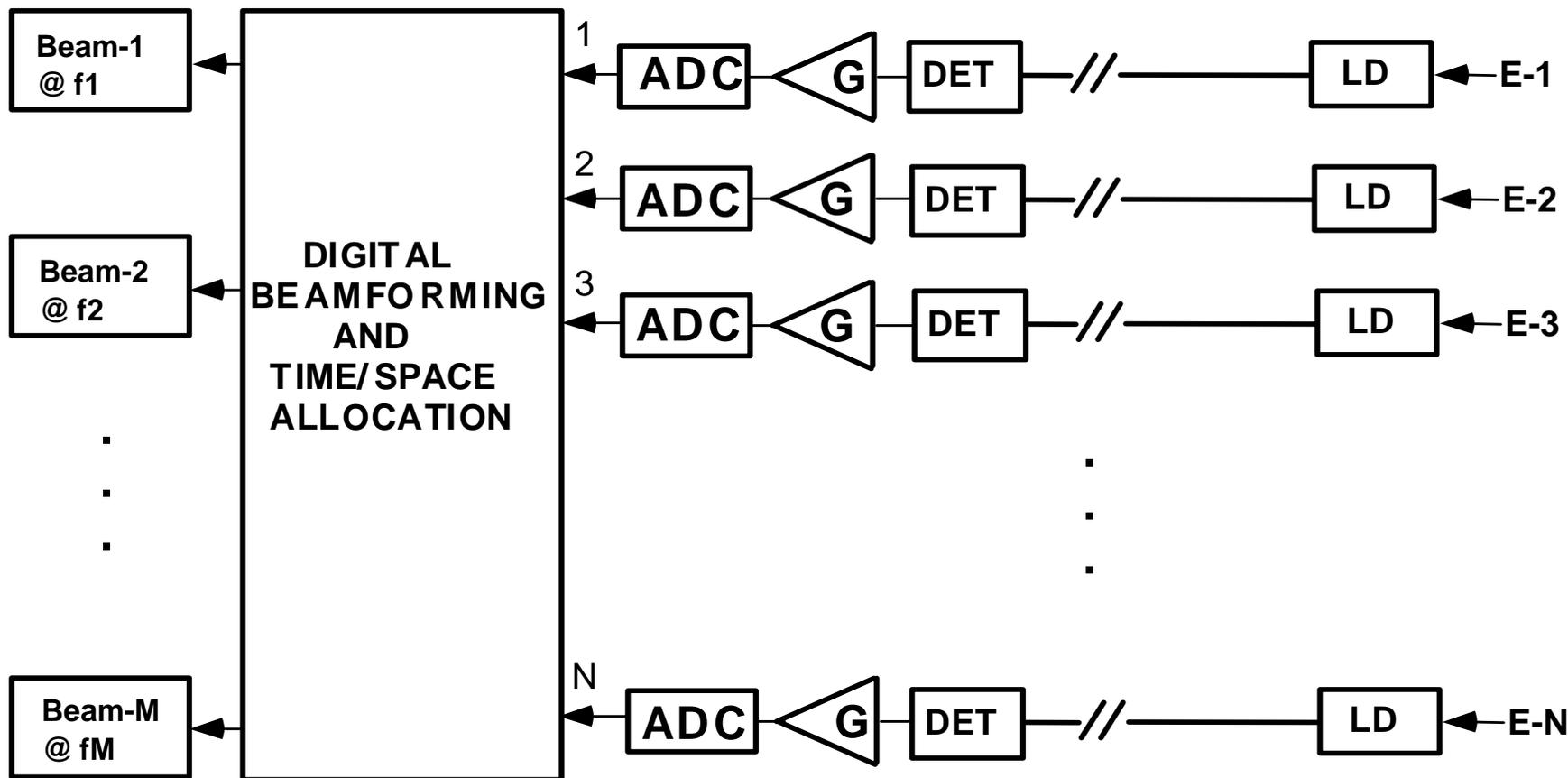

For DBF, STAP algorithms require $\sim N^3$ digital computations

Need: Low loss optical delay lines (DBF/RF manifolds)

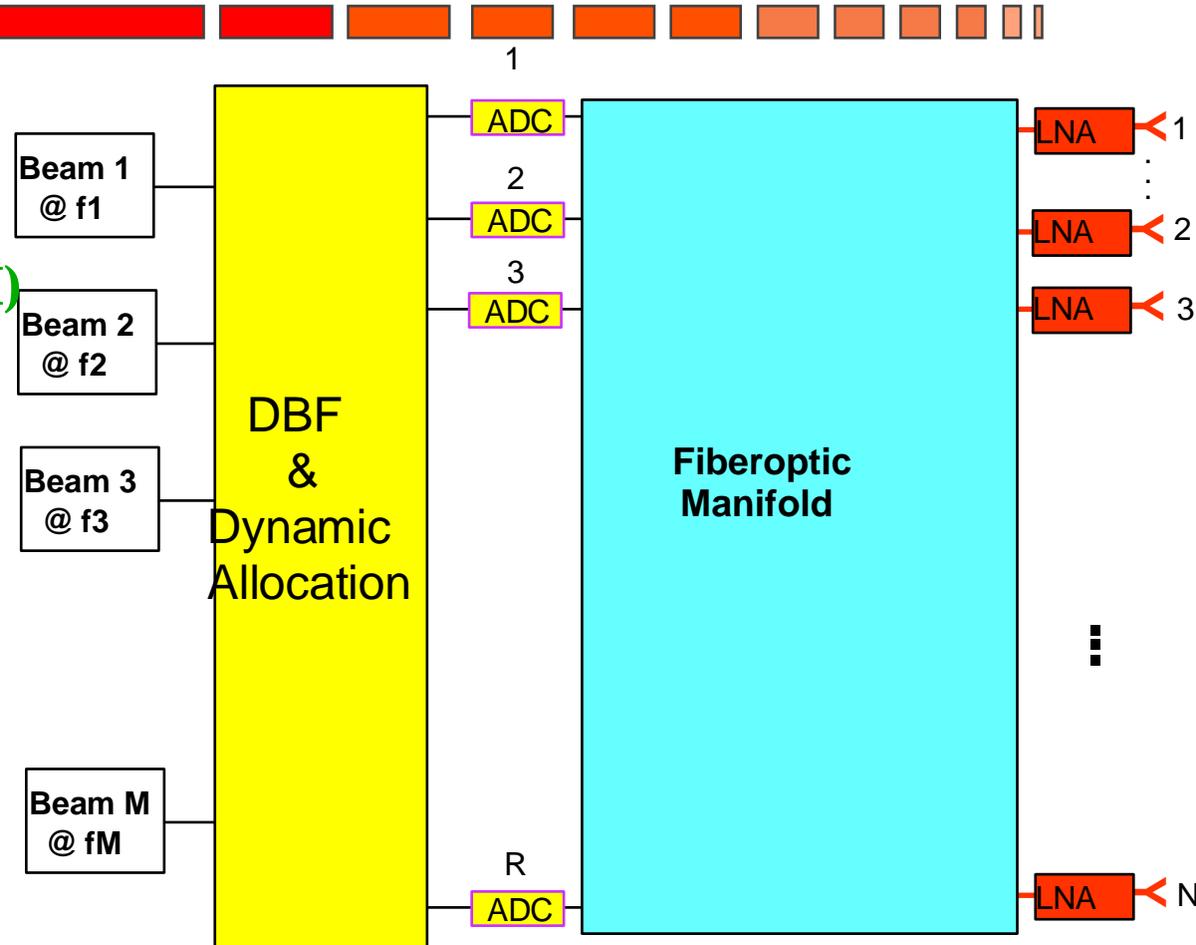- DBF forms M beams from R Manifolds ($N > R > M$)
- ADCs needed: R not M
- Less digital computation:




Example: STAP with $N=1000$, $R=50$, $M=10$

No FO manifold: 10×1000^3 computations


With FO manifold: 10×50^3 computations (8×10^3 LESS !!!)

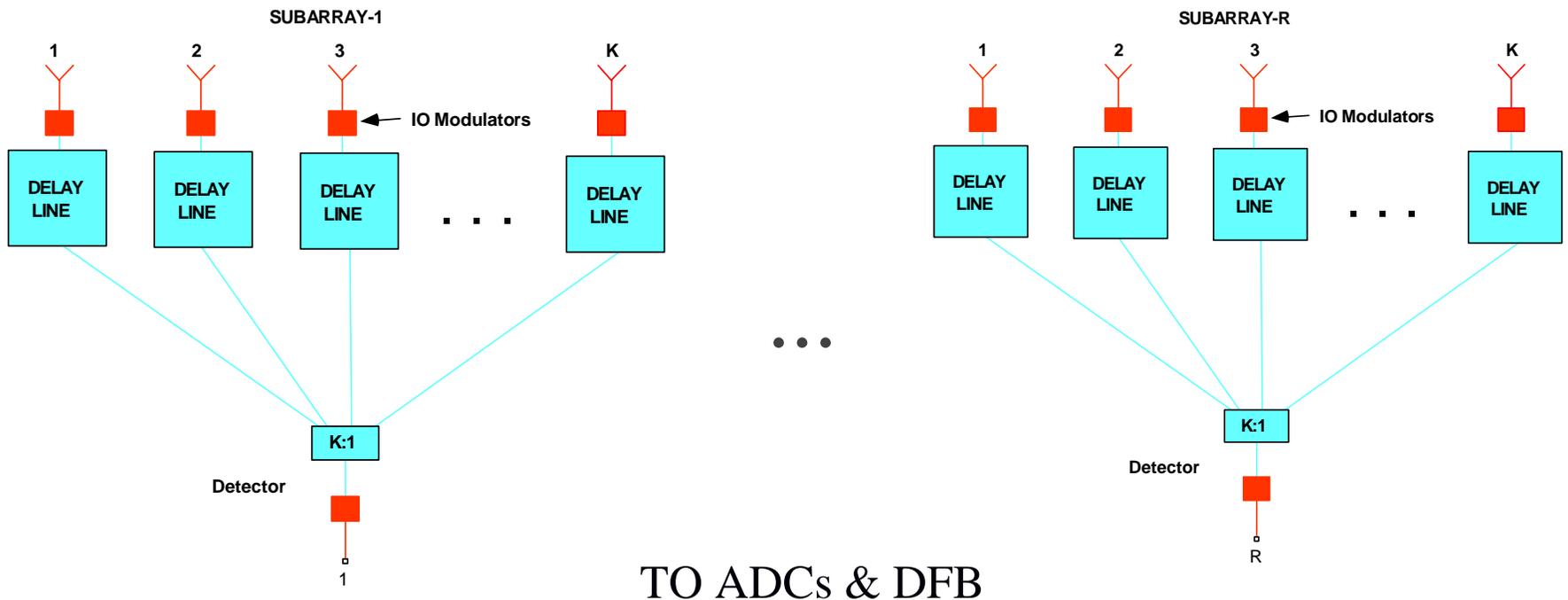Need: *Low loss optical delay lines (DBF/RF manifolds)*




- Sub-array level analog optical manifolds will be needed for many current and future DFB applications
- Key element needed is a low cost, programmable delay line (4 bits OK)

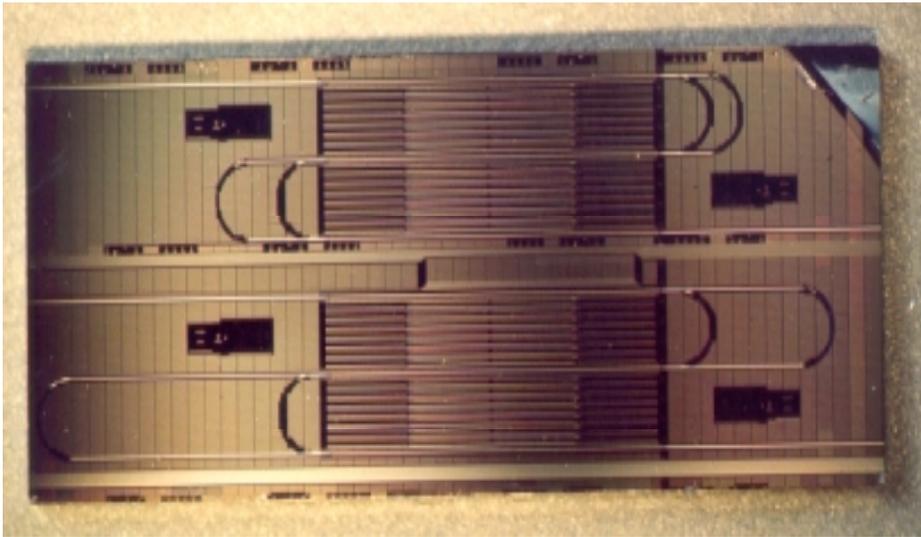Binary Photonic Delay Line: *Examples of previous work*




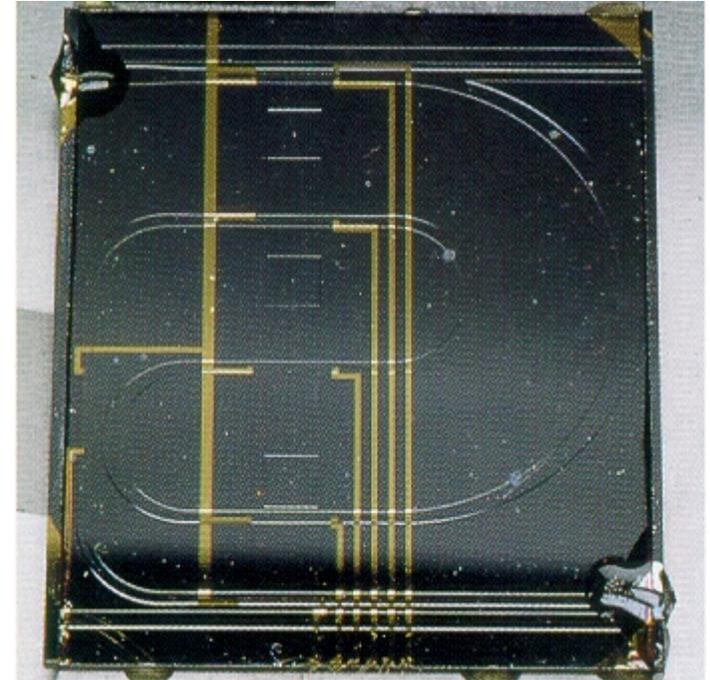- Honeywell 3-bit, Integrated Optical BIFODEL in GaAs
Delays: 250, 176, 83 ps, Size: 25x12.5x1 mm
- Loss= 16.1 dB for 3 bits




- NOI 5-bit, Integrated Optical BIFODEL in Silica
Total delay is ~ 1 ns (20 cm path)
- Loss= 20 dB for 5 bits

Navy AMRFS Architecture

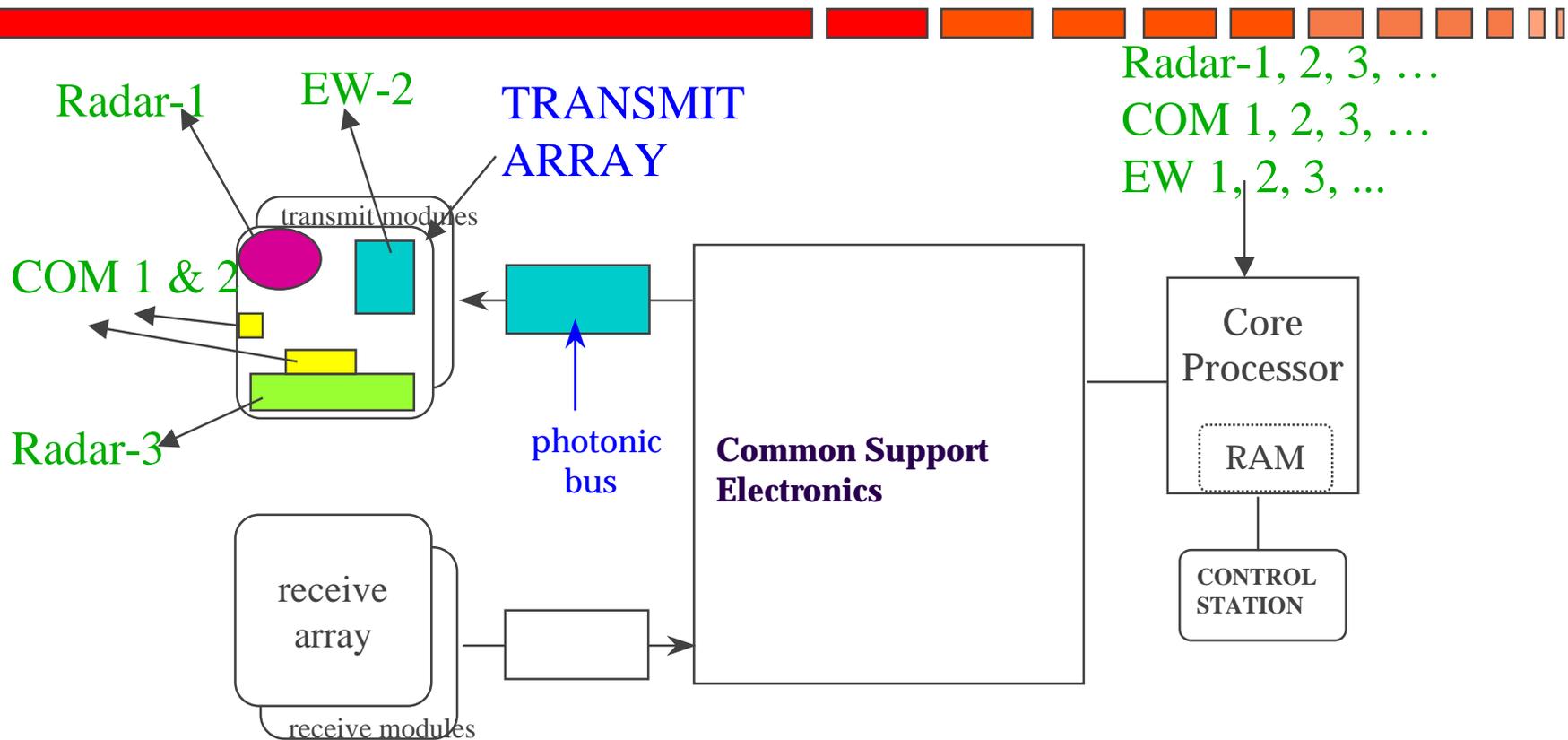

Effective dynamic allocation of wideband multifunction apertures and transmit/receive resources requires an advanced RF interconnection network, with programmable *broadcast, multicast, and narrowcast* capability.

Need: *Optical tunable filters*

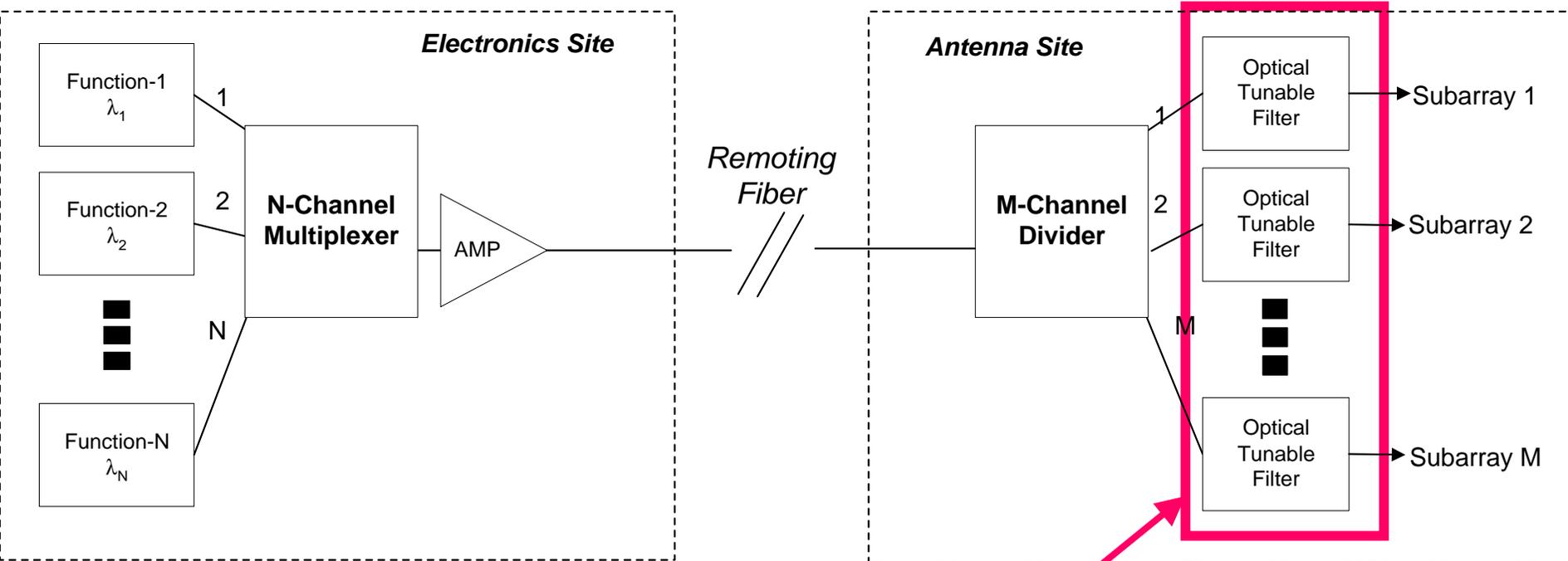

Need: *Optical tunable filters*



BW: 29.6 nm (vs 14 nm of bus)
3 dB Op. BW: 0.15 nm (18.75 GHz)
IL: 3.0 dB, Speed: 50 nm/ms



BW: 30 nm (vs 14 nm of bus)
0.5 dB Op. BW: 0.6 nm (75 GHz)
IL: 1.0 dB, Speed: Manual

- **COTS filters drift, are lossy, and affect the system Phase Noise**
- **Need: low cost stable tunable filter bank (size is not an issue)**
(1 ms speed, 0.5-dB optical BW of 0.6 nm, 1-2 dB loss)